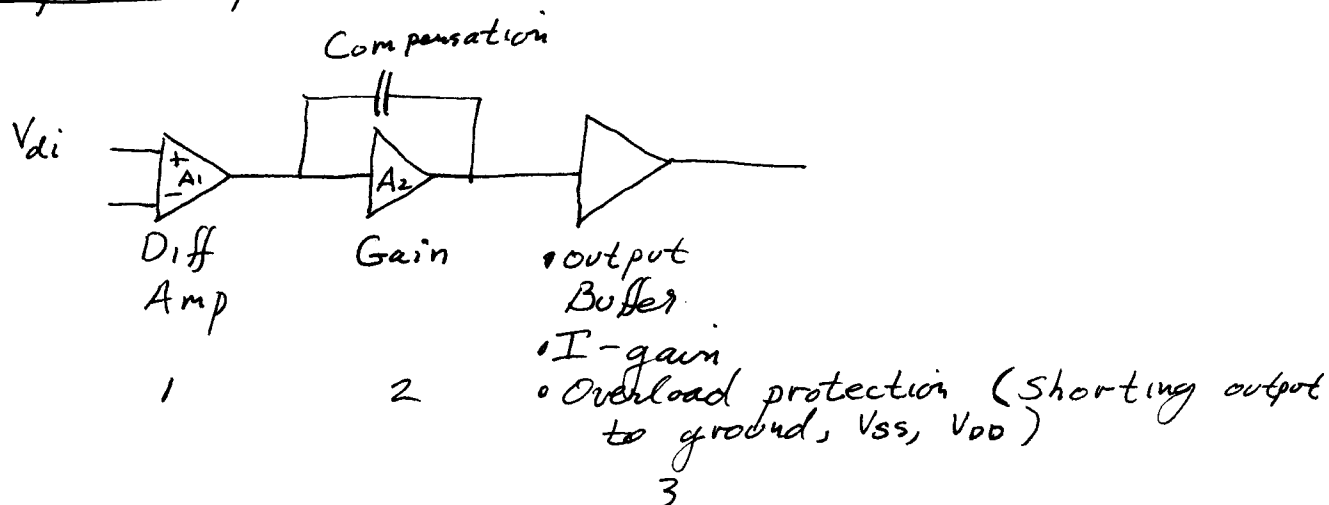


CH 25Op AmpsFIG. 25.20. Current Mirror I-Source $m5$ & $m6$. I_{ss} bias current1. Diff Amp with active load (Fig p 9.1)(a) Source coupled pair $m1$ & $m2$ (b) Active load $m3$ & $m4$

(c) Gain of diff amp



$$A_1 = g_{m1} (r_{o2} \parallel r_{o4})$$

$$= \frac{2 \sqrt{\beta_1}}{(\lambda_2 + \lambda_4) \sqrt{I_{ss}}}$$

$$= \frac{2}{(\lambda_2 + \lambda_4) (V_{GS} - V_{THN})}$$

W6

9.1

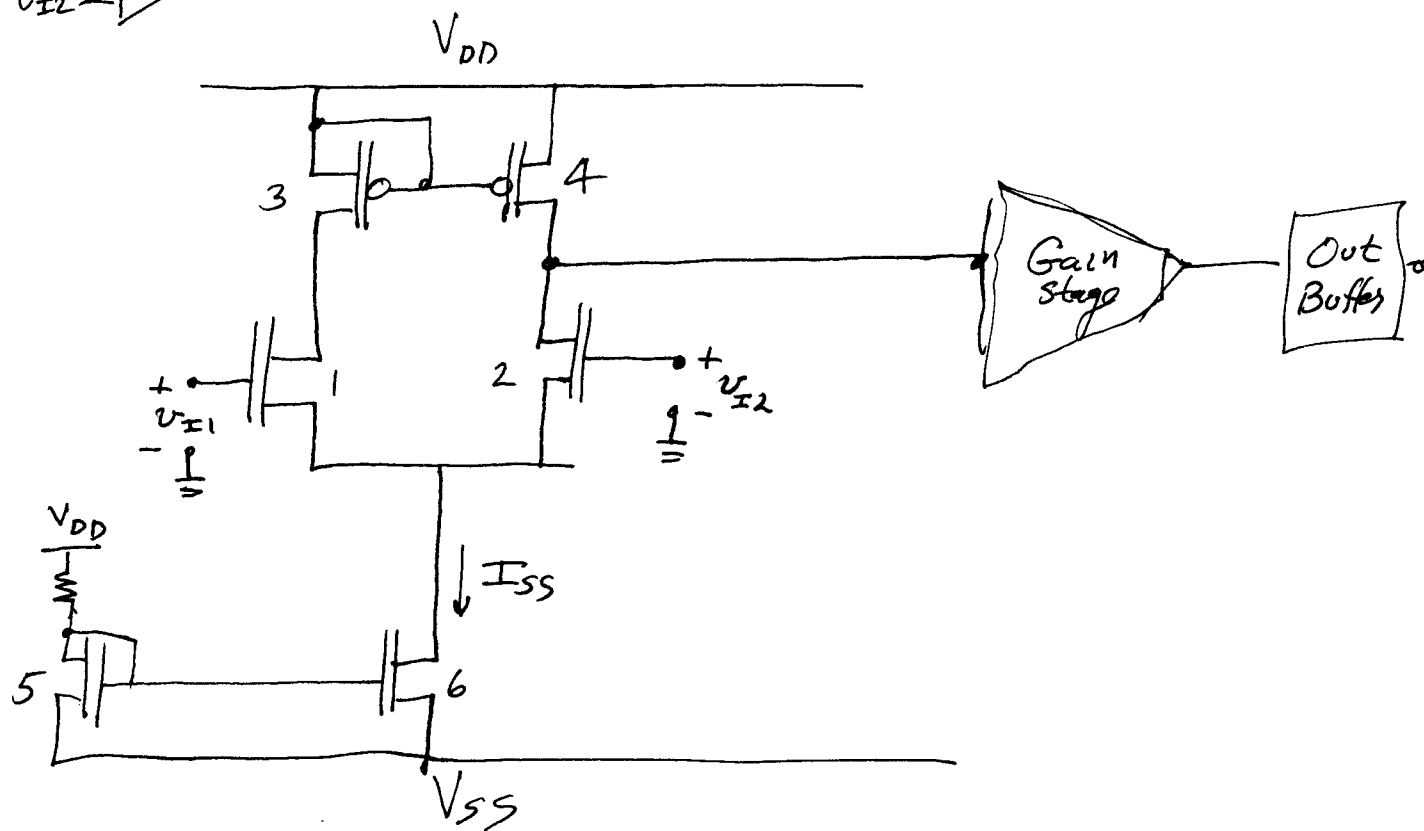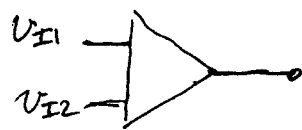

(d) Design Considerations

$$\begin{aligned} \uparrow \frac{W}{L} &\Rightarrow \downarrow V_{GS} \Rightarrow \uparrow CMR \Rightarrow \text{better matching} \\ &\Rightarrow \uparrow \text{gain} \\ &\Rightarrow \uparrow \text{parasitic } C_s \Rightarrow \downarrow f_{-3dB} \end{aligned}$$

(e) For off-chip use, $W \approx 200 \mu\text{m}$ range

2. Gain Stage (Fig. P11)

(a) Single stage common source (~~PMOS~~) amp (M7) with active load (M8)

(b) M9 & M10 provide voltage drop of $2 V_{GS}$.

(c) BIASING

* SIZING M7

$$\text{For } V_{I1} = V_{I2} = 0$$

$$\left. \begin{aligned} I_{SS}/2 \text{ flows thru } M3 \text{ \& } M4 \\ \text{Also } V_{GS3} = V_{GS4} \end{aligned} \right\} \Rightarrow V_{SD3} = V_{SD4} = V_{SG3,4}$$

$$\Rightarrow V_{SD4} = V_{SD3} = V_{SG3,4}$$



$$\Rightarrow V_{SG7} = V_{SG3,4}$$

$$\text{For } I_{D7} = I_{SS}/2 \text{ choose } \left(\frac{W}{L}\right)_7 = \left(\frac{W}{L}\right)_{3,4}$$

* SIZING M8

$$\text{Choose } \left(\frac{W}{L}\right)_8 \text{ s.t. } I_{D8} = I_{D7}.$$

(d) Gain (low f) (Ignore C_c)

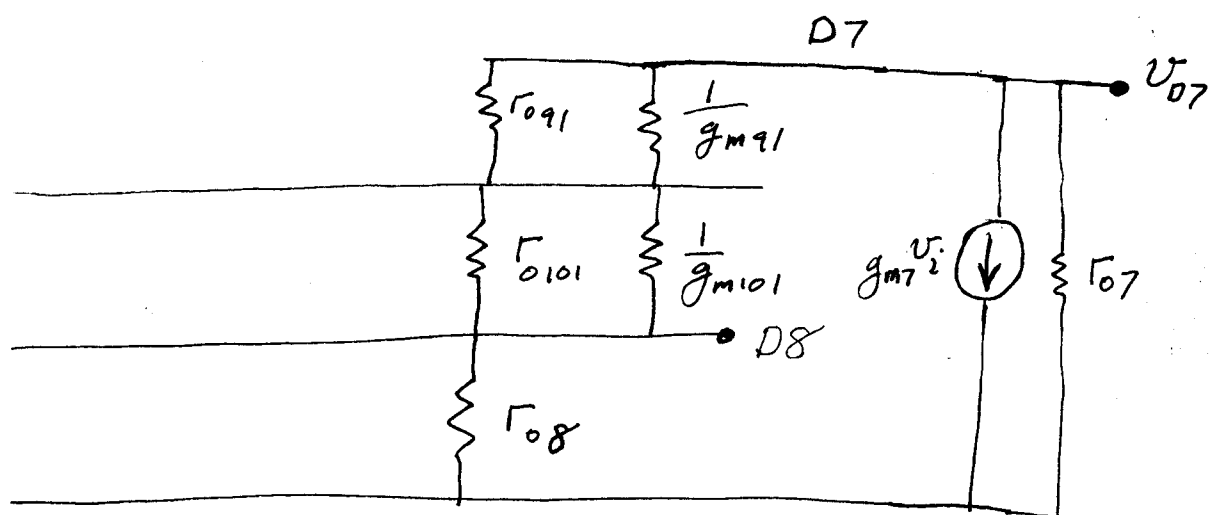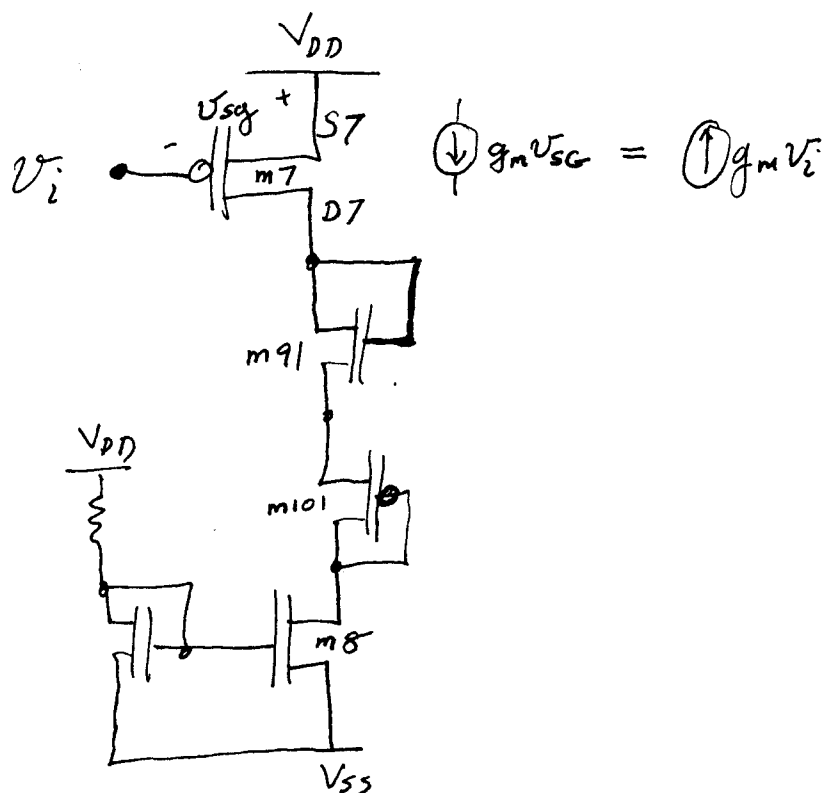

$$\frac{v_{o7}}{v_i} = -g_{m7} \left[r_{o8} + \underbrace{\left(r_{o10} \parallel \frac{1}{g_{m10}} \right)}_{1/g_m} + \underbrace{\left(r_{o9} \parallel \frac{1}{g_{m9}} \right)}_{1/g_m} \right] \parallel r_{o7}$$

$$\approx -g_{m7} r_{o8} \parallel r_{o7}$$

$$v_{D8} = v_{D7} \frac{r_{o8}}{r_{o8} + \frac{1}{g_{m101}} + \frac{1}{g_{m11}}} \approx v_{D7} \frac{r_{o8}}{r_{o8}} = v_{D7}$$

$$\begin{aligned} A_{v2} &= -g_{m7} (r_{o7} \parallel r_{o8}) \\ &= \frac{-\sqrt{2\beta_7}}{(\lambda_7 + \lambda_8)\sqrt{I_{D7}}} = \frac{-2\sqrt{\beta_7}}{(\lambda_7 + \lambda_8)\sqrt{I_{ss}}} \\ &= \frac{-2}{(\lambda_7 + \lambda_8)(V_{SG1} - V_{THP})} \end{aligned}$$

(e) Open Loop Gain A_{OL}

$$A_{OL} = A_{v1} A_{v2} =$$

$$\begin{aligned} &= -g_{m1} g_{m7} (r_{o2} \parallel r_{o4}) (r_{o7} \parallel r_{o8}) \\ &= \frac{-4\sqrt{\beta_1 \beta_7}}{(\lambda_2 + \lambda_4)(\lambda_7 + \lambda_8) I_{ss}} \end{aligned}$$

$$\left(\text{for } \left(\frac{W}{L}\right)_7 = \left(\frac{W}{L}\right)_4 \quad (I_{D7} = I_{ss}/2)\right)$$

$$\text{FOR } I_{ss} = 10 \mu A$$



$$\beta_1 = \frac{1}{2} 50 \frac{\mu A}{V^2} \left(\frac{15}{5}\right)$$

$$\beta_7 = \frac{1}{2} 17 \frac{\mu A}{V^2} \frac{70}{5}$$

$$\lambda_2 = \lambda_4 = \lambda_7 = \lambda_8 = 0.06 \frac{1}{V}$$

$$\begin{aligned} A_{OL} &= 2600 \quad (\text{typical order of magnitude}) \\ A_{OL}(I_{ss} = 1 \mu A) &= 26,000 \end{aligned}$$

3. Output Stage Class AB

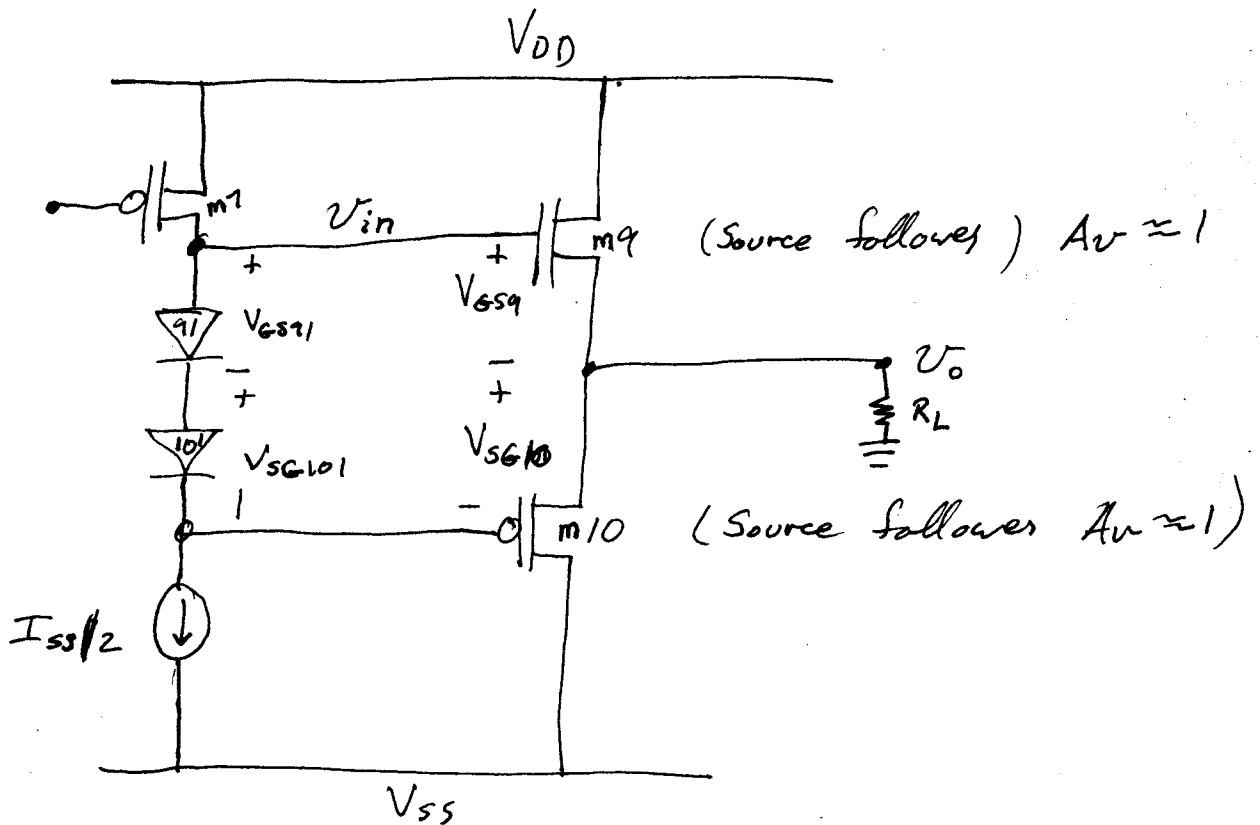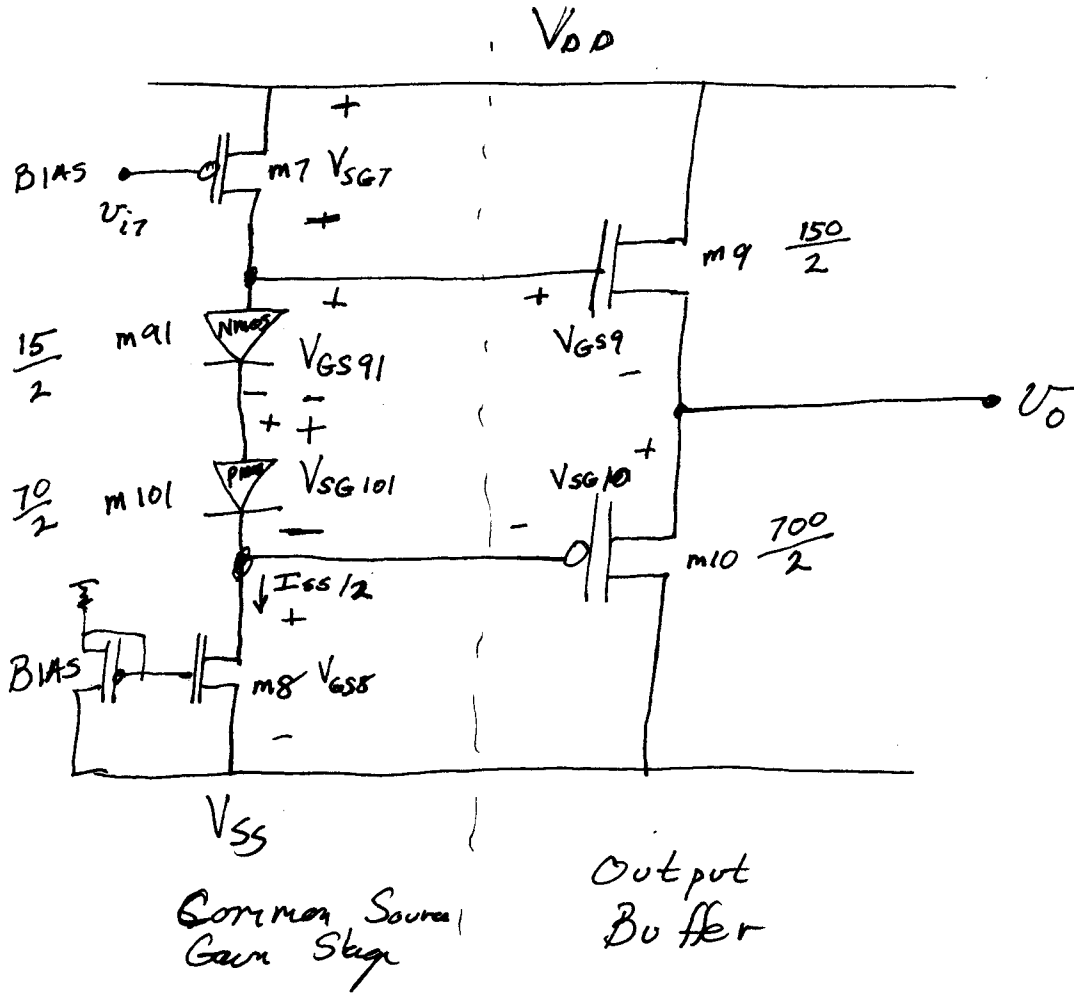

With no ac signal, $v_{i7} = 0$

$$I_{D7} = I_{SS}/2 = I_{D91} = I_{D101}$$

$$V_{GS9} + V_{SG10} = V_{GS91} + V_{SG101} = \text{fixed}$$


~~Choose~~ Choose $(W/L)_{9,10}$

$\Rightarrow$ m_9 & m_{10} are biased on w/ current dependent on $\frac{W}{L}$ ratios.

- As v_{g9} goes $(-)$ $\downarrow$, ~~m_9 forces v_o to follow~~


$$\left. \begin{array}{l} V_{GS9} \downarrow \\ V_{SG10} \uparrow \end{array} \right\} V_{GS9} + V_{SG10} = \text{const.}$$

For negative v_{g9}

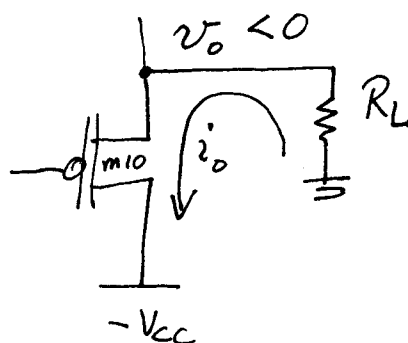

Output current flows thru m_{10}

- For $+ v_{g9}$

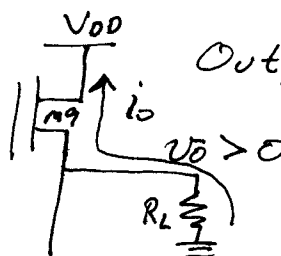

Output flows thru m_9 .

W7

0

$$V_{G9 \text{ max}} = V_{DD} \iff V_{SD7} = 0 = V_{SG7} - V_{THP}$$

$$V_{G10 \text{ min}} = V_{SS} \iff V_{DS8} = 0 = V_{GS8} - V_{THN}$$

• Choose a max $|V_{GS}| = 1.2 \text{ V}$

$$\implies V_{OUT \text{ max}} = V_{DD} - 1.2$$

$$V_{OUT \text{ min}} = V_{SS} + 1.2$$

$$I_{OUT \text{ max}} = \frac{\beta_9}{2} (V_{GS9} - V_{THP})^2 =$$

$$= 50 \frac{\mu\text{A}}{\text{V}^2} \frac{150}{2} (1.2 - 0.83)^2 = 500 \mu\text{A}$$

$$I_{O \text{ min}} = \frac{\beta_{10}}{2} (V_{SG10} - V_{THP})^2 = 17 \frac{\mu\text{A}}{\text{V}^2} \frac{700}{2} (1.2 - 0.91)^2 = 500 \mu\text{A}$$

OVERLOAD PROTECTION

What happens when $V_{G9} = V_{DD}$ & V_O is shorted to V_{SS} ?

For $V_{DD} = |V_{SS}| = 2.5 \text{ V}$,


$$V_{GS9} = 5 \text{ V}$$

$$I_O = 65 \text{ mA}$$

$$P_9 = 0.065 (5) = 0.33 \text{ W}$$

How to keep ^{max} V_{GS9} & max $V_{SG10} \lesssim 1.2 \text{ V}$?

OVERLOAD PROTECTION

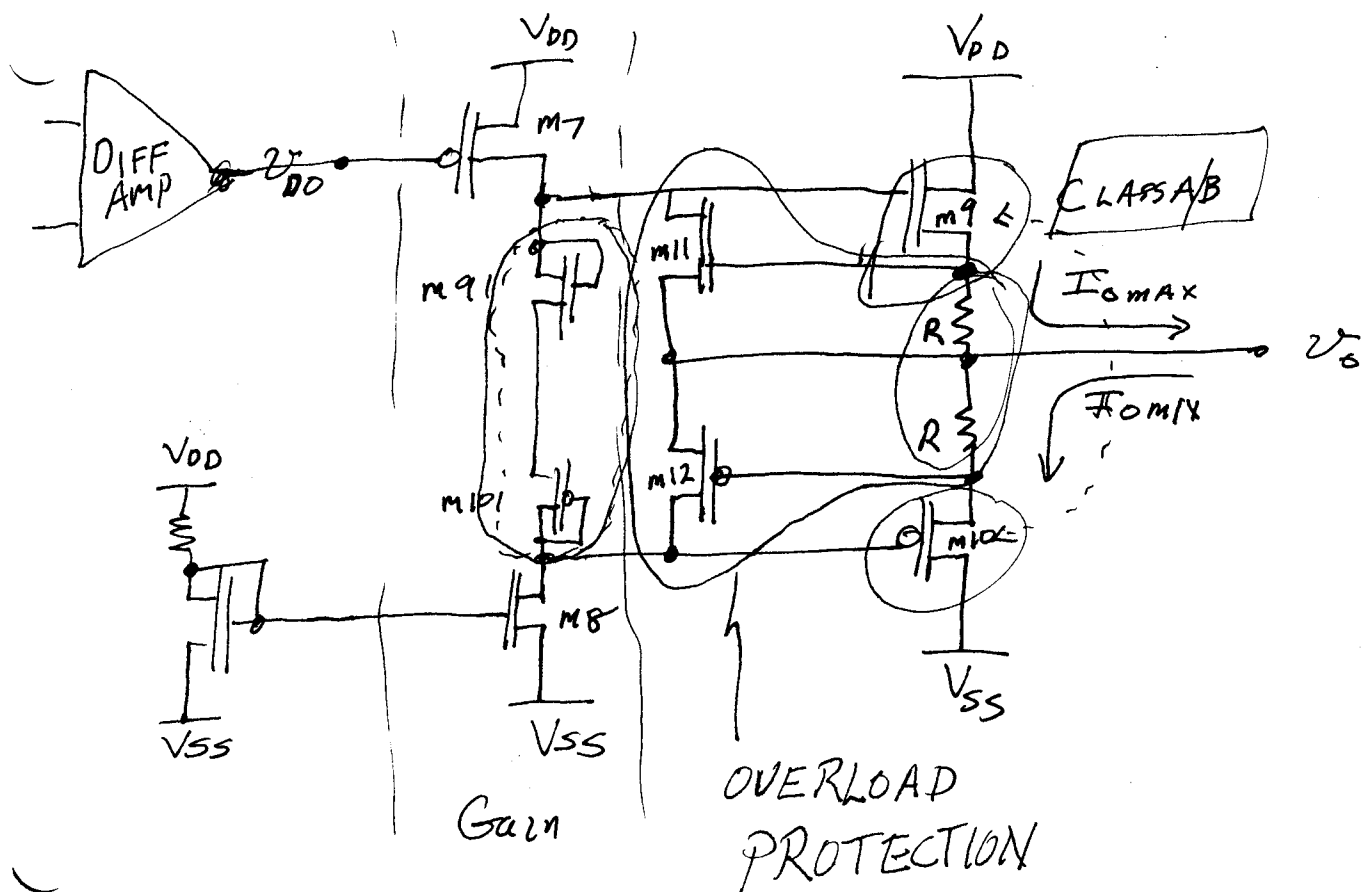

- When $I_{Omax} = \frac{V_{THN}}{R}$, $m11$ turns on
 $\Rightarrow$ Pulls $V_{G9} \downarrow$ & shuts off $m9$
- When $I_{Omin} = \frac{V_{THP}}{R}$, $m12$ turns on
 $\Rightarrow$ Pulls $V_{G10} \uparrow$ & shuts off $m10$.


Choose $R = 1 \text{ k}\Omega$

$1 \text{ mA} \cdot 1 \text{ k}\Omega = 1 \text{ V} \Rightarrow m11 \text{ on}$
 pulling V_{G9} down to V_O .

W7 FREQUENCY RESPONSE & COMPENSATION 7

- Op - Amps Always used in feedback configuration.

STABILITY OF FEEDBACK AMP

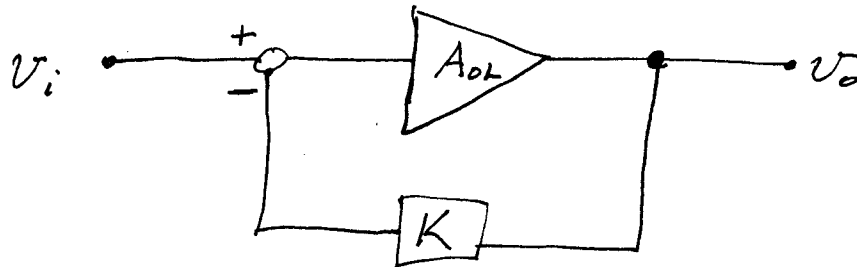


$$A_{CL} = \frac{A_{OL}}{1 + KA_{OL}}$$

Unstable when $KA_{OL} = -1 \Rightarrow A_{CL} = \infty$

$$KA_{OL} = -1 \iff |KA_{OL}| = 1 \text{ \& } \angle KA_{OL} = \pm 180^\circ$$

$$\text{MAX } K = 1.$$

$\Downarrow$

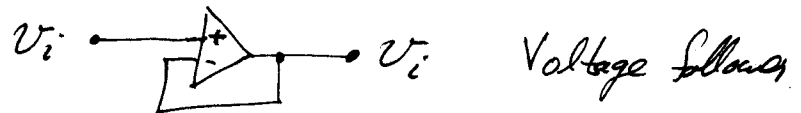


Voltage follower

Unstable if $|A_{OL}| \geq 1$ when $\angle A_{OL} = \pm 180^\circ$


COMPENSATION

To adjust $|A_{OL}|$ & $\angle A_{OL}$ for stable
unity feedback (Worst case scenario)

FREQUENCY RESPONSE & COMPENSATION

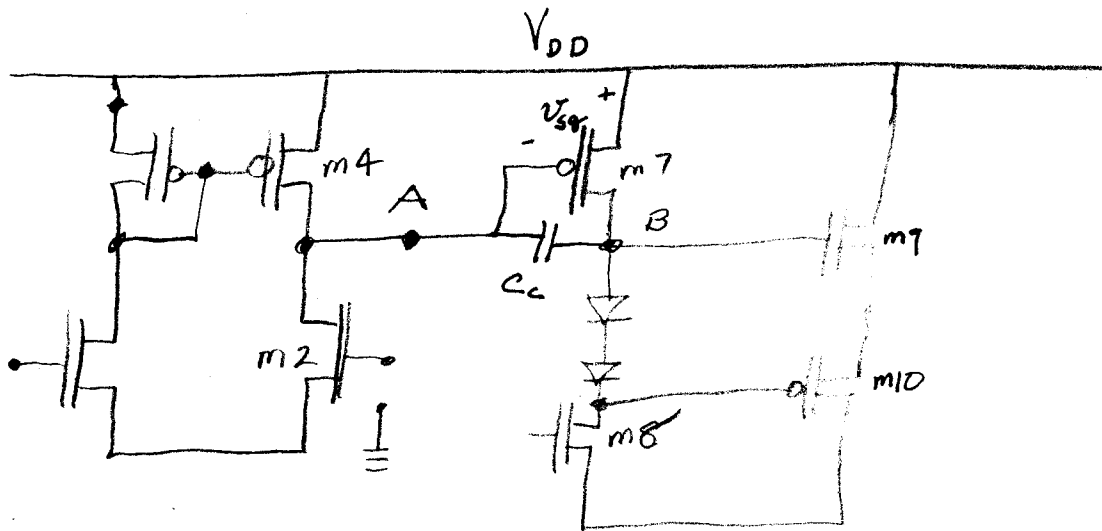

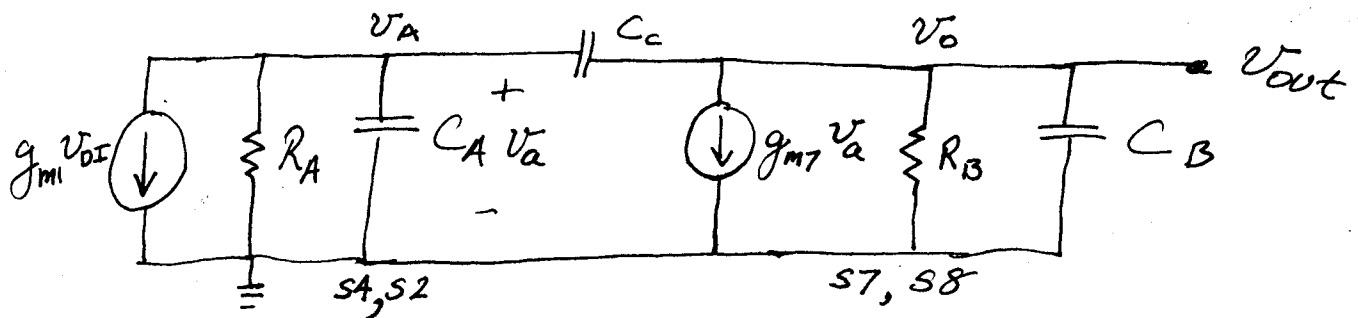DOMINANT POLES AT High impedance nodes.
 NODE A: OUTPUT OF DIFF AMP



Calc $T_1 = R_A C_A$


$$R_A = r_{o2} \parallel r_{o4} = \frac{1}{(\lambda_2 + \lambda_4) \frac{I_{SS}}{2}} = \frac{1}{(0.06 + 0.06)(10e-6)} = 833.33 k\Omega$$

$$C_A = \underbrace{(C_{db4} + C_{gd4} + C_{db2} + C_{gd2})}_{\text{DIFF AMP } C_{out}} + \underbrace{C_L}_{\text{Due to } m7}$$

$$C_L = C_{gs7} + C_{gd7} (1 + |A_{v2}|)$$

$$C_{db2} = C_{j0} \cdot 6\mu\text{m} \cdot 15\mu\text{m} = 9.4 \text{ fF}$$

$1e-4 \frac{\text{pF}}{\mu\text{m}^2}$

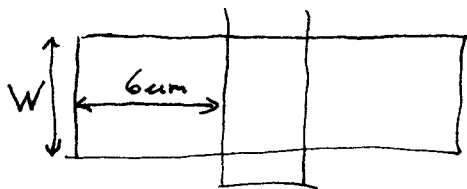

$$C_{db4} = C_{j0} \cdot 6\mu\text{m} \cdot 70\mu\text{m} = 137 \text{ fF}$$

$$C_{gd2} = CGDO_{NMOS} \cdot W_2 = 3.8e-10 \cdot 15\mu\text{m} = 5.7 \text{ fF}$$

$$C_{gd4} = CGDO_{PMOS} \cdot W_4 = 5e-10 \cdot 70\mu\text{m} = 35 \text{ fF}$$

$$C_{gs7} = \frac{2}{3} \cdot C_{ox} \cdot W_7 L_7 =$$

$$= \frac{2}{3} \cdot 7.94e-16 \cdot 70 \cdot 5 = 1.85e-13 \text{ F}$$

$(\frac{\text{F}}{\mu\text{m}^2})$ $= 185 \text{ fF}$

$$C_{gd7} = CGDO_{PMOS} W = 5e-10 \frac{\text{F}}{\text{m}} 70\mu\text{m}$$

$\uparrow$ $= 35 \text{ fF}$

$(t_{ox} = 4.35e-8 \text{ m})$

• Multiply by miller effect

$$|A_{v2}| = \frac{+2\sqrt{\beta_7}}{(\lambda_7 + \lambda_8)\sqrt{I_{SS}}} = \frac{2\sqrt{\frac{1}{2} 17 \frac{\mu\text{A}}{\text{V}^2} \cdot \frac{70}{5}}}{(0.06 + 0.06)\sqrt{10\mu\text{A}}}$$

$$= 57.5$$

$$C_{gd7} (1 + 57.5) = \frac{2.05 \text{ pF} = 2047 \text{ fF}}{= C_{M7}} \quad \text{Miller Cap.}$$

$$C_{gs7} + C_{gd7} (1 + 57.5) = 2232 \text{ fF}$$

$$C_A = \frac{+ 187}{2.42 \text{ pF}}$$

$$\tau_1 = R_A C_A = 2.017 \mu\text{s}$$

$$f_1 = \frac{1}{2\pi\tau_1} = 78.9 \text{ kHz}$$

W7

4

$$\text{CALC } \tau_2 = R_B C_B$$

$$R_B = r_{o7} \parallel r_{o8} = R_A = 833 \text{ k}\Omega$$

$$C_2 = C_{gd7} + C_{db7} + C_{db8} + C_{gd8} + \underbrace{(C_{gd9} + C_{gd10})}_{\text{Output Buffers}}$$

$\uparrow$ $C_{gd7} \left(1 + \frac{1}{A_{v7}}\right) = C_{gd7}$ $\uparrow$
 C_{gd7} appears in C_1 & C_2 .

$$C_2 = \underbrace{35 \text{ fF} + 137 \text{ fF} + 9.4 \text{ fF} + 5.7 \text{ fF}}_{\text{Gain Stage } m7 + m8} = 187.1 \text{ fF}$$

$$+ 3.8 \times 10^{-10} \frac{\text{F}}{\text{m}} \cdot 150 \mu\text{m} = 57 \text{ fF} \quad (C_{gd9})$$

$$+ 5 \times 10^{-10} \frac{\text{F}}{\text{m}} \cdot 700 \mu\text{m} = 350 \text{ fF} \quad (C_{gd10})$$

$$C_2 = 594 \text{ fF}$$

$$\tau_2 = 0.495 \mu\text{s}$$

$$\boxed{f_2 = \frac{1}{2\pi\tau_2} = 321 \text{ kHz}}$$

$$\frac{1}{1+j\omega RC} = \frac{1}{1+j2\pi f RC}$$

$$= \frac{1}{1+j \frac{f}{1/2\pi RC}}$$

UNITY GAIN f

$$A_v = \frac{A_{vo}}{(1+j \frac{f}{f_1})(1+j \frac{f}{f_2})} \quad (A_{vo} = 2600)$$

$$|A_v| = \frac{A_{vo}}{\left(1 + \left(\frac{f}{f_1}\right)^2\right)^{1/2} \left(1 + \left(\frac{f}{f_2}\right)^2\right)^{1/2}} = 1$$

$$A_{vo}^2 = \left(1 + \left(\frac{f}{f_1}\right)^2\right) \left(1 + \left(\frac{f}{f_2}\right)^2\right)$$

$$A_{vo}^2 \approx \frac{f^4}{f_1^2 f_2^2} \quad f = \sqrt{f_1 f_2 A_{vo}}$$


$$= 8.1 \text{ MHz}$$

SPICE $\Rightarrow$ 20 MHz

PHASE

$$A_v = A_{vo} \frac{(1 - j \frac{f}{f_1})(1 - j \frac{f}{f_2})}{[1 + (\frac{f}{f_1})^2][1 + (\frac{f}{f_2})^2]}$$
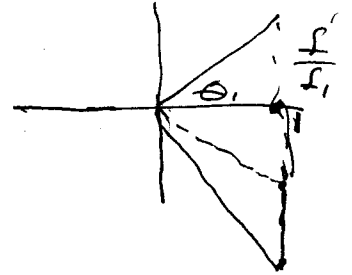
$$A_{vo} R_1 e^{i\theta_1} R_2 e^{i\theta_2} = R_1 R_2 e^{i(\theta_1 + \theta_2)}$$



$$\theta_1 = -\text{atan} \frac{f}{f_1}$$

$$\theta_2 = -\text{atan} \frac{f}{f_2}$$

$$\theta_1 + \theta_2 =$$

$$\text{@ } f = 8.1 \text{ MHz} \quad \theta_1 = -\text{atan} \frac{8100}{78.9} = -89^\circ$$

$$\theta_2 = -\text{atan} \frac{8100}{321} = -87^\circ$$

$$\theta_1 = -89^\circ$$

$$\theta_2 = -87^\circ$$

$$\left. \begin{array}{l} \theta_1 = -89^\circ \\ \theta_2 = -87^\circ \end{array} \right\} \theta_1 + \theta_2 = -176^\circ$$

$\Rightarrow$ NO PHASE MARGIN!

FOR STABILITY, WANT


$$|\theta| \leq$$

$$|\angle A_v| \leq 135^\circ \text{ @ } |A_v(f)| = 1$$

$$\equiv \underline{45^\circ \text{ Phase Margin}}$$

WHY?
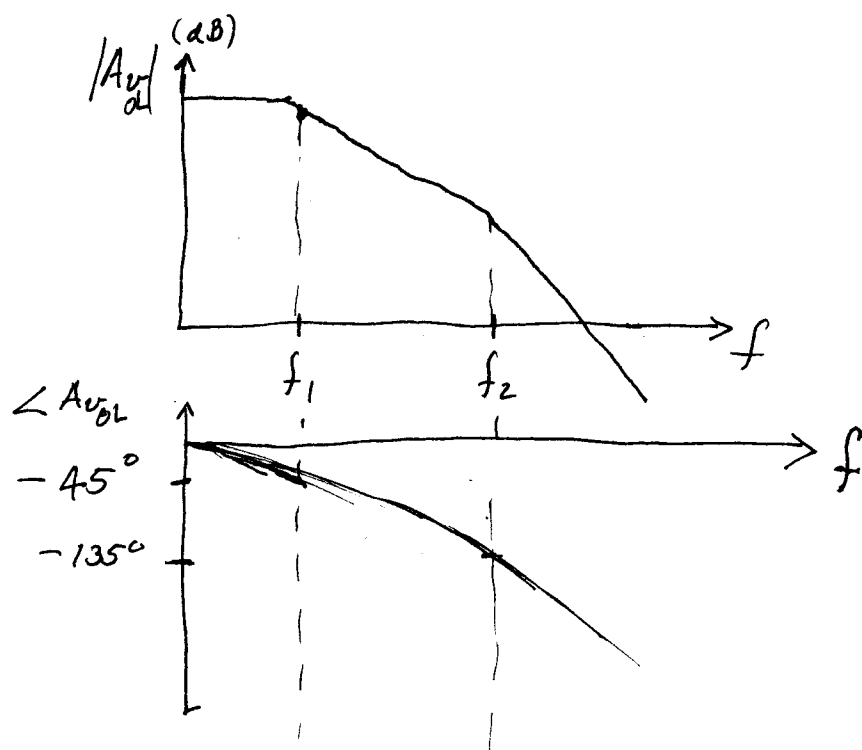
$$A_v(f) = \frac{A_{vo} (1 - j\frac{f}{f_1})(1 - j\frac{f}{f_2})}{(1 + (\frac{f}{f_1})^2)(1 + (\frac{f}{f_2})^2)}$$



If $|A_v| > 1$ when $\angle A_v$ reaches 180° ,
 $\Rightarrow$ poles in RHP (s-plane)

$$\frac{A_{voL}(s=0)}{(1 - \frac{s}{p_1})(1 - \frac{s}{p_2})}$$

For $p_{1,2} = \sigma \pm j\omega$ with $\sigma > 0$

$A_v(t) \approx e^{\sigma t} \sin \omega t \rightarrow$ unstable or oscillatory.