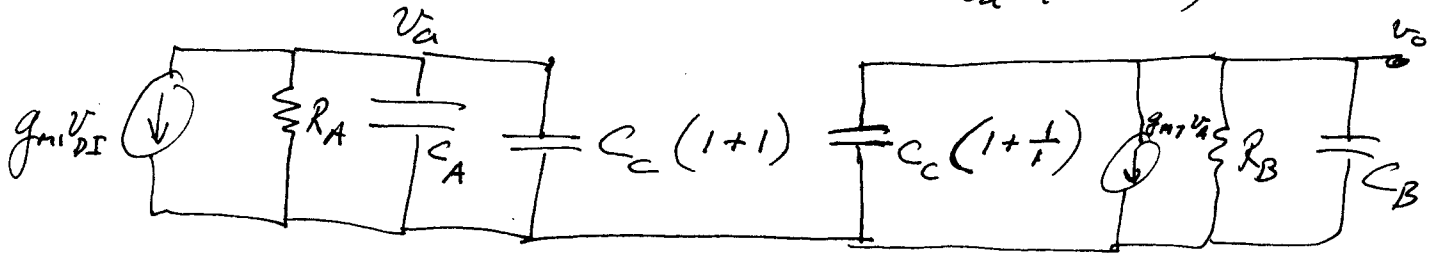


COMPENSATE W/ CAP C_c

~~At ω~~

CHOOSE C_c

At unity gain C_c act as a short
so that $v_{out} = v_a$. ($|\frac{v_{out}}{v_a}| = 1$)



$$v_a = \frac{g_{m1} v_{DI}}{j\omega C_c (2)} \quad (v_o - v_a) j\omega C_c$$

$$v_o = -\frac{g_{m7} v_a}{j\omega C_c (2)} = -\frac{g_{m1} g_{m7} v_{DI}}{\omega^2 C_c^2 4}$$

$$\left| \frac{v_o}{v_{DI}} \right| = 1 = \frac{g_{m1} g_{m7}}{4 \omega_u^2 C_c^2} \quad (g_{m1} \approx g_{m7})$$

$$\frac{g_{m1}}{2 \omega_u C_c} = 1$$

$$\frac{g_{m1}}{4 \pi f_u} = C_c$$

↑ book uses 2

W7


8

Choose f_u to give $\geq 45^\circ$ phase margin.

Setting $f_u = 1 \text{ MHz}$

$$C_c = \frac{55 \mu\text{A}/V^2}{2\pi 10^6 (\frac{1}{2})} = 8.75 \text{ pF}$$

$$f_{-3dB} =$$

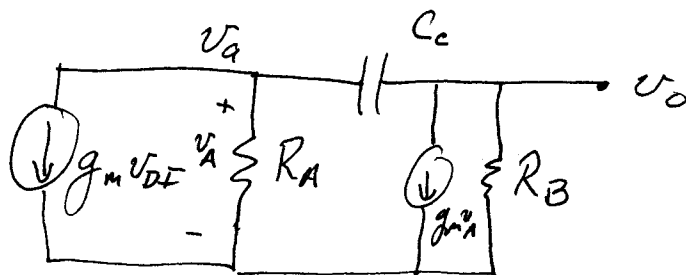


$$(v_o - v_a) j\omega C_c = g_m v_{DI} + \frac{v_a}{R_A}$$

$$\tau_A = R_A \parallel C_c (1 + A_{v2})$$

$$8.75 \text{ pF} (58.5) 833 \text{ k}\Omega = 0.043 \text{ s}$$

$$f_{-3\text{dB}} = 23 \text{ Hz}$$

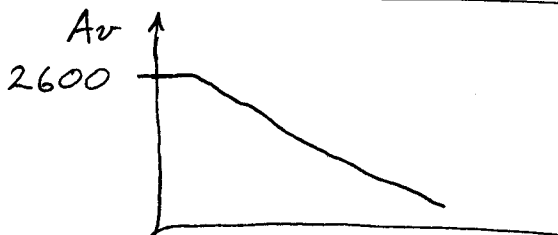

Zero

$$g_m v_{DI} + \frac{v_a}{R_A} = \frac{v_o - v_a}{j\omega C_c}$$

$$g_m v_a + \frac{v_o}{R_B} + (v_o - v_a) j\omega C_c = 0$$

$$(g_m - j\omega C_c) v_a + v_o \left(\frac{1}{R_B} + j\omega C_c \right) = 0$$

$$v_a = v_o \left(\frac{\frac{1}{R_B} + j\omega C_c}{j\omega C_c - g_m} \right)$$

$$g_m v_{DI} + v_o \left(\frac{\frac{1}{R_B} + j\omega C_c}{j\omega C_c - g_m} \right) \frac{1}{R_A} = v_o \left[1 - \frac{\frac{1}{R_B} + j\omega C_c}{j\omega C_c - g_m} \right]$$

$$g_{m1} v_{DI} = v_o j\omega C_c \bar{v}_a \left(\frac{1}{R_A} + j\omega C_c \right)$$

$$g_{m1} v_{DI} = v_o j\omega C_c - v_o \frac{\frac{1}{R_B} + j\omega C_c}{j\omega C_c - g_{m7}} \left(\frac{1}{R_A} + j\omega C_c \right)$$

$$g_{m1} v_{DI} = v_o \left[s C_c - \frac{1}{R_B g_{m7}} \frac{1 + s C_c R_B}{(-1 + s C_c / g_{m7})} \frac{1}{R_A} (1 + s R_A C_c) \right]$$

$$= v_o \left[\frac{+1}{R_A R_B g_{m7}} \right] \left[s C_c R_A R_B g_{m7} + \frac{(1 + s R_B C_c)(1 + s R_A C_c)}{(1 - s C_c / g_{m7})} \right]$$

$$= \frac{v_o}{R_A R_B g_{m7}} \left[\frac{s C_c R_A R_B g_{m7} - s^2 C_c^2 R_A R_B + (1 + s R_B C_c)(1 + s R_A C_c)}{1 - s C_c / g_{m7}} \right]$$

$$\frac{v_o}{v_{DI}} = \frac{g_{m1} g_{m7} R_A R_B (1 - s C_c / g_{m7})}{(1 + s R_B C_c)(1 + s R_A C_c) + s C_c R_A R_B g_{m7} - s^2 C_c^2 R_A R_B}$$

in RHP:

$$\text{Zero} = z = \frac{g_{m7}}{C_c} = s, \text{ or } f_z = \frac{g_{m7}}{2\pi C_c}$$

$$\text{Recall } f_u \approx \frac{g_{m1}}{2\pi C_c}$$

Zero adds phase & reduces roll-off.

$\Rightarrow$ reduces phase margin.

Intuitively,

C_c shorts v_a to v_o


$$\Rightarrow v_o = -g_{m1} v_{DI} \frac{R_A}{1 + j\omega R_A C_c} \approx +g_{m1} v_{DI} \frac{(j)}{\omega}$$

$$= -\frac{A_{vDO}}{j\omega R_A C_c} =$$

W7

11

MOVE ZERO by adding R_Z

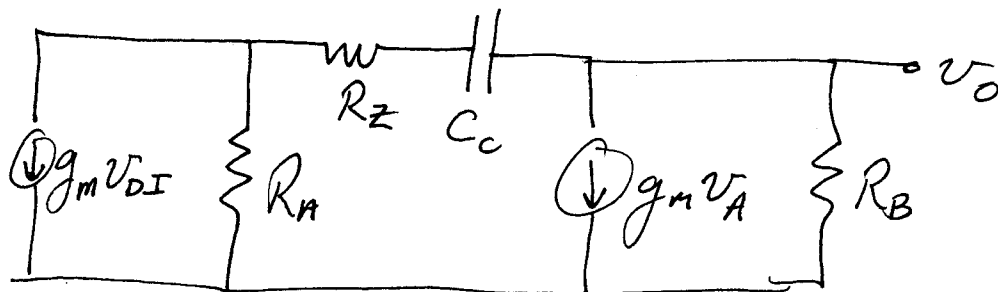

$$\Rightarrow \frac{1}{sC_c} \rightarrow \frac{1}{sC_c} + R_Z$$

$$\text{or } sC_c \rightarrow \frac{sC_c}{1 + sR_Z C_c}$$

$$1 - \frac{sC_c}{g_m} \rightarrow 1 - \frac{sC_c}{g_m(1 + sR_Z C_c)}$$

$$\frac{1}{g_m(1 + sR_Z C_c)} [g_m + sR_Z C_c - sC_c]$$

$$g_m \left[1 + s(R_Z C_c - \frac{C_c}{g_m}) \right]$$

$$\left[1 + sC_c(R_Z - \frac{1}{g_m}) \right]$$

$$\left[1 - sC_c(\frac{1}{g_m} - R_Z) \right]$$

$$Z = \frac{1}{C_c(\frac{1}{g_m} - R_Z)}$$




For $R_Z > \frac{1}{g_m}$ $Z \rightarrow \text{LHP}$

$\&$ Z adds to phase margin (Good)

$R_Z = \frac{1}{g_m}$ zero gone.

$\rightarrow \text{W8 p.0.1}$


W8

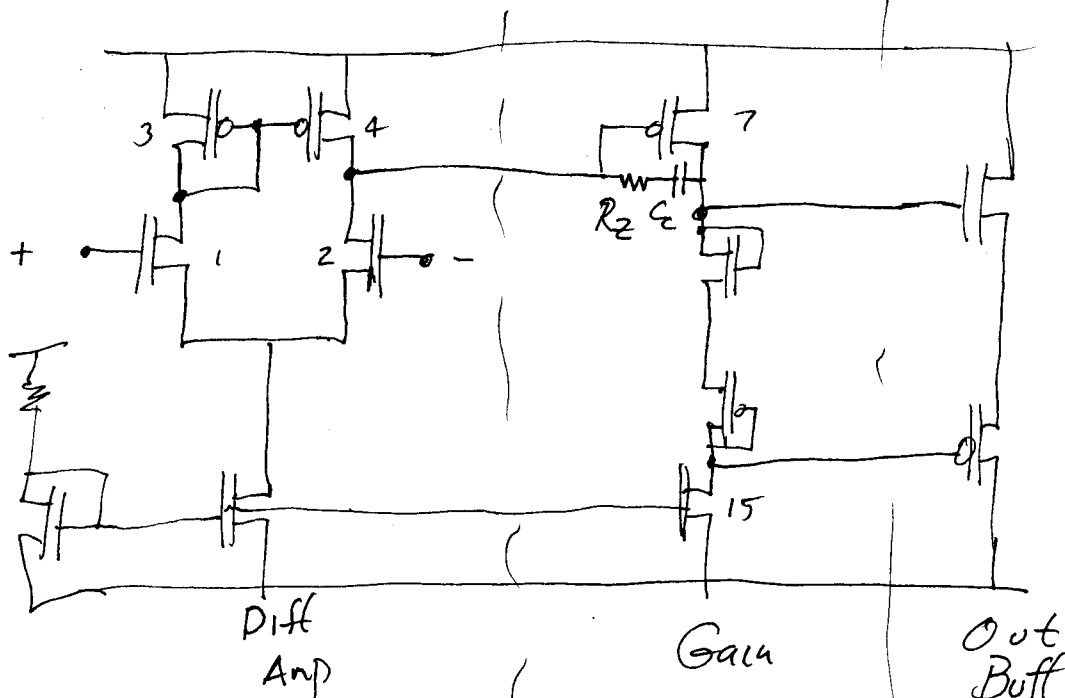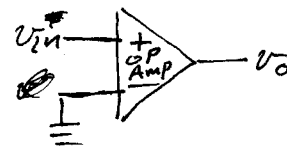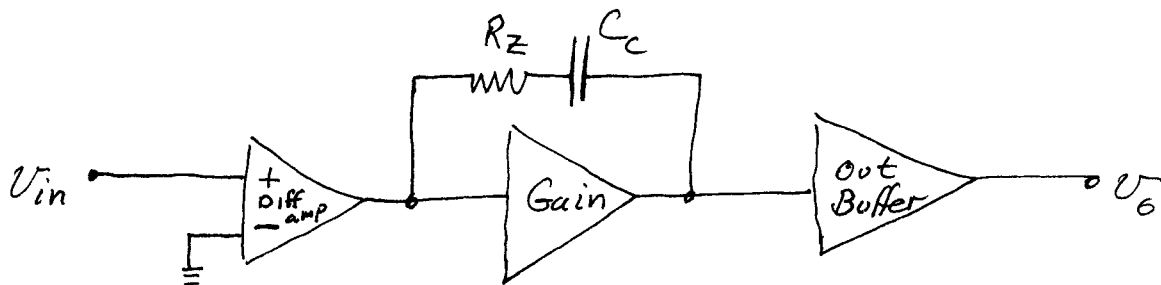

→ 0.1
RZ

BASIC Topology of OP AMP

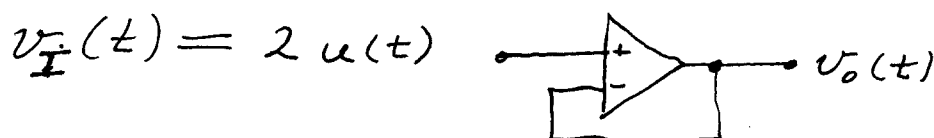- So far discussed small signal f-response.
- What about SLEW RATE?
- Consider op-amp in unity gain (voltage follower) configuration w/



- Assume response dominated by a single pole:

$$\frac{V_o}{V_i}(s) = \frac{A=1}{1+s\tau}$$

$$v_o(s) = \frac{2}{s} \cdot \frac{1}{1+s\tau} = \frac{2}{s} - \frac{2}{s+1/\tau}$$

$$v_o(t) = 2(1 - e^{-t/\tau}) u(t) \quad (\text{WRONG})$$

ACTUALLY response is linear

- $v_o(t)$ is determined by how fast you can charge C_c .

$$v_o(t) = \frac{I_{ss}}{C_c} t$$


Only I_{ss} from diff-amp is available to charge C_c .

→ p. 0.2W8

IMPLEMENTING R_Z w/ transistor

$\Rightarrow R_Z$ can track $\frac{1}{g_{m7}}$ over Temp. & process variations

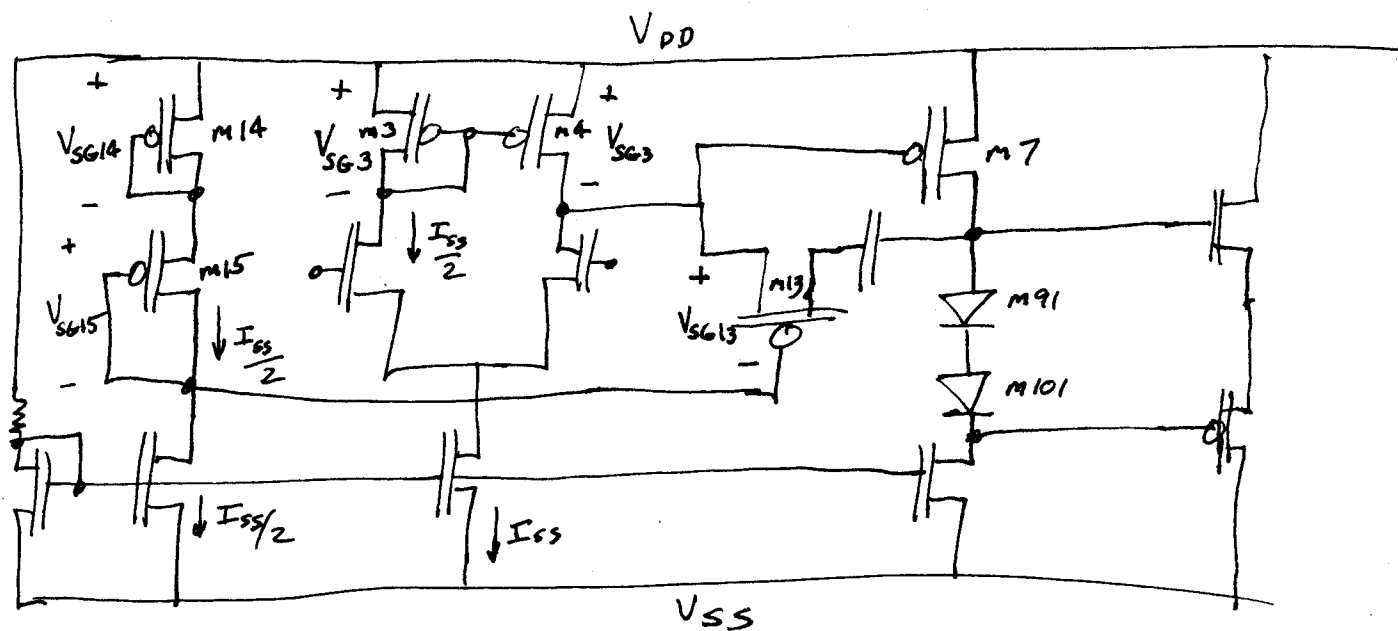(To get rid of zero, want $R_Z = 1/g_{m7}$)



DC BIASING of M13

$$V_{SG13} = \overbrace{V_{DD} - V_{SG3}}^{V_{S13}} - (\overbrace{V_{DD} - V_{SG14} - V_{SG15}}^{V_{SG3}}) \\ = V_{SG3} \quad (W_{14} = W_{15} = W_3 = W_4)$$

- $V_{SG3} > V_{THP} \Rightarrow$ not cutoff $\Rightarrow$ triode w/ $V_{SD} = 0$
- $I_{SD13} = 0 \Rightarrow V_{SD13} = 0$

$$I_{SD13} = \beta_{13} \left[(V_{SG3} - V_{THP}) V_{SD13} - \frac{V_{SD13}^2}{2} \right]$$

$$\left. \frac{\partial I_{D13}}{\partial V_{SD13}} \right|_{V_{SD13}=0} = \underbrace{\beta_{13} (V_{SG3} - V_{THP})}_{g_{m7}} = \frac{1}{R_Z}$$

~~W8 P. 10~~

W8

0.2

$$V_{SG7} = V_{SG3}$$

$$g_{m7} = \beta_7 (V_{SG3} - V_{THP})$$

$$\text{FOR } \beta_7 = \beta_{13}, \quad R_Z = \frac{1}{g_{m7}} \Rightarrow \text{zero } \text{removed.}$$


$$\text{Want } R_Z > \frac{1}{g_{m7}}, \text{ choose } W_{13} < W_7.$$

$$R_Z = \frac{L_{13}}{W_{13} \mu_p C_{ox} (V_{SG3} - V_{THP})}$$

→ P.O

FIGURES of MERIT of OP-AMP

1) Input offset voltage

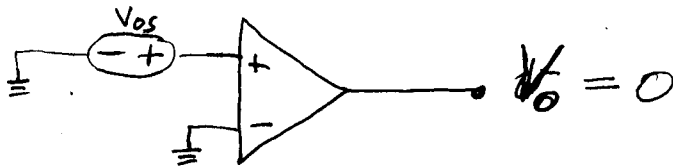


$V_{OS} = V_{IN}$ required to drive $V_O = 0$.
WORST CASE:

$$V_{OS} = \frac{V_{DD}}{A_{OL}} \text{ or } \frac{V_{SS}}{A_{OL}}$$

$$\frac{V_{SS}}{A_{OL}} \leq V_{OS} \leq \frac{V_{DD}}{A_{OL}}$$

2/2

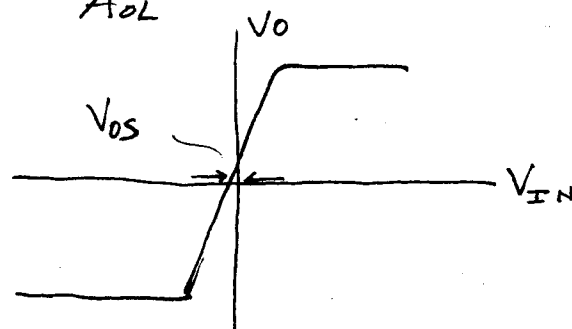

2) OUTPUT V-SWING (Determined by class A/B OUT Buffer)

$$\left[V_{DD} - |V_{GS\text{MAX}}| \right] - \left[V_{SS} + |V_{GS\text{MAX}}| \right]$$


$$= V_{DD} - V_{SS} - 2|V_{GS\text{MAX}}| \quad (\text{MAX VALUE})$$

(ACTUALLY LESS)

- Determined by linear part of V_o vs.

V_{IN} curve

(SPICE)

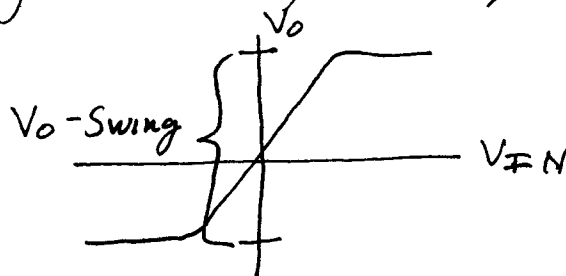

3) Common Mode Rejection Ratio (CMRR)

$$CMRR = 20 \log_{10} \left(\frac{A_{OL}}{A_c A_2} \right) \quad \text{open Loop Gain}$$

Common Mode
Gain of Diff Amp

Gain of gain stage

$$= 20 \log_{10} \left(\frac{A_1 A_2}{A_c A_2} \right) = 20 \log_{10} \frac{A_1}{A_c}$$

$$= CMRR \text{ of Diff-Amp.}$$

NB: ^{ONLY} The diff amp discriminates betⁿ differential V_{IN} & common V_{IN} .

4) Power Dissipation

$$\underbrace{(V_{DD} - V_{SS})}_{5V} (\text{TOTAL DC CURRENT})$$


$$(I_{D5} + I_{D6} + I_{D8} + I_{D10})$$

$$\frac{I_{SS}}{2} \quad I_{SS} \quad \frac{I_{SS}}{2} \quad \frac{I_{SS}(10)}{2} =$$

$$I_{SS} \left(\frac{1}{2} + 1 + \frac{1}{2} + 5 \right) = 0.14 \text{ mA}$$

$$= 5V (0.00014 \text{ A}) = \underline{0.7 \text{ mW}}$$

5) Power Supply Rejection Ratio

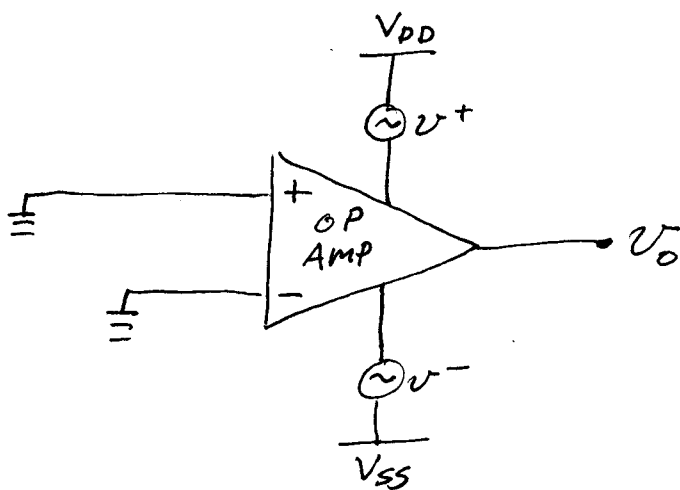

$$PSRR^+ = \frac{A_{OL}}{\underbrace{v_o / v^+}_{A_p}}$$

$$PSSR^- = \frac{A_{OL}}{v_o / v^-}$$

6) Slew rate

← P.D